


Digital Logic Design

Hajar Falahati


Department of Computer Engineering
IRAN University of Science and Technology

hfalahati@iust.ac.ir






Flip Flops

 

Positive edge sensitive flip-flop

 

Negative edge sensitive flip-flop

   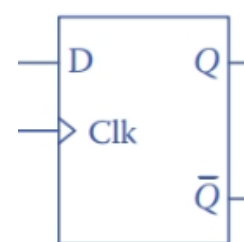 

	R	S	Q	$\bar{Q}$
Hold the value	0	0	Q	$\bar{Q}$
Set the value	0	1	1	0
Reset the value	1	0	0	1
Invalid	1	1	Invalid	

	J	K	Q	$\bar{Q}$
Hold the value	0	0	Q	$\bar{Q}$
Reset the value	0	1	0	1
Set the value	1	0	1	0
Toggle the value	1	1	$\bar{Q}$	Q


D	Q	$\bar{Q}$
0	0	1
1	1	0

Delay FF


T	Q	$\bar{Q}$
0	Q	$\bar{Q}$
1	$\bar{Q}$	Q

Hold the value
Toggle the value


Modeling

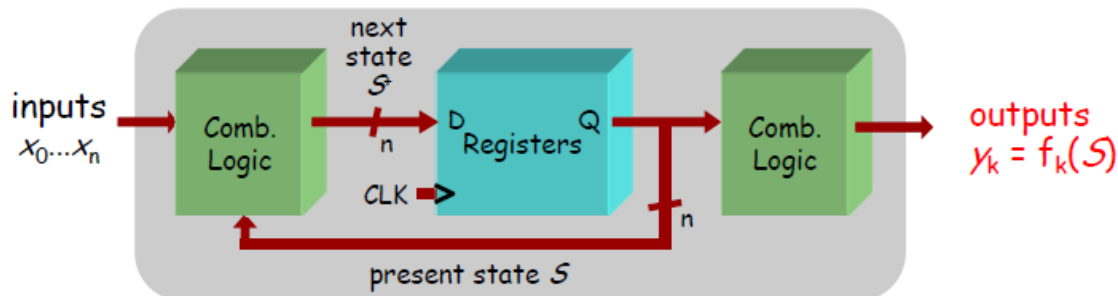

Moore FSM

 

Mealy FSM

 

Outline


- Synthesis of Synchronous Sequential Circuits




Synthesis

Synthesis

 
- Design a sequential circuit
- Steps
 - Specification of the required behavior
 - Create state diagram/state table
 - Determine the number of flipflops
 - Determine the type of flipflops
 - Find combinational logic to produce output
 - Find combinational logic to produce next state



Sequential Circuit: Specification

 

(a) Completely specified circuit

 


(b) Incompletely specified circuit

Synthesis: State Assignment

- Assign codes to each state

- A : 00
- B : 01
- C : 11
- D : 10

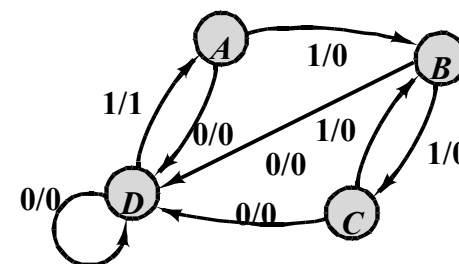

State	Q ₁	Q ₂	Q ₃
0	0	0	0
1	1	0	0
2	1	1	0
3	1	1	1
4	0	1	1
5	0	0	1

State	y ₁	y ₂
A	0	0
B	0	1
C	1	1
D	1	0


State Assignment

	x	
	0	1
A	A/0	B/0
B	A/0	C/1
C	B/0	D/0
D	C/1	D/0

State Table

Synthesis: Input Assignment

 - Assign codes to each input
- Already done here!



State	y_1	y_2
A	0	0
B	0	1
C	1	1
D	1	0



State Assignment

	x	
	0	1
A	A/0	B/0
B	A/0	C/1
C	B/0	D/0
D	C/1	D/0

State Table

Synthesis: Input Assignment: Sample

  
- Assign codes to each input
 - U:1
 - D:0



CBA	$C+B+A$	
	U	D
000	001	111
001	010	000
010	011	001
011	100	010
100	101	011
101	110	100
110	111	101
111	000	110

Synthesis: Output Assignment

 - Assign codes to each output
- Already done here



State	y_1	y_2
A	0	0
B	0	1
C	1	1
D	1	0

State Assignment


	x	
	0	1
A	A/0	B/0
B	A/0	C/1
C	B/0	D/0
D	C/1	D/0

State Table

Synthesis: Input Assignment: Sample


- Assign codes to each output

- a: 00
- b: 01
- c: 11

 

Synthesis: Transition Table

 - Output: $z = g(x, y)$
- Excitation: $Y = h(x, y)$



	x	
	0	1
A	A/0	B/0
B	A/0	C/1
C	B/0	D/0
D	C/1	D/0

State Table

State	y_1	y_2
A	0	0
B	0	1
C	1	1
D	1	0

State Assignment

		x	
		0	1
$y_1 y_2$			
00		00/0	01/0
01		00/0	11/1
11		01/0	10/0
10		11/1	10/0

$Y_1 Y_2/z$

Transition Table

Synthesis: Output Simplification

- Simplifies output
 - Output: $z = g(x, y)$

$y_1 y_2$		x	
		0	1
00	0	0	0
01	0	1	
11	0	0	
10	1	0	

z

$y_1 \ y_2$		x	
		0	1
00	00/0	01/0	
01	00/0	11/1	
11	01/0	10/0	
10	11/1	10/0	

$$z = x\bar{y}_1y_2 + \bar{x}y_1\bar{y}_2$$

Synthesis: Transistor Selection

- Determine the number and types of Flip flops

- Excitation: $Y = h(x, y)$
- Number of states
- Two FF
- Select D

		x	
		0	1
$y_1 y_2$	00	00/0	01/0
	01	00/0	11/1
	11	01/0	10/0
	10	11/1	10/0
		$Y_1 Y_2/z$	

State transitions		Required inputs
$Q(t)$	$Q(t + e)$	$D(t)$
0	0	0
0	1	1
1	0	0
1	1	1

(a) D flip-flop

State transitions		Required inputs	
$Q(t)$	$Q(t + e)$	$S(t)$	$R(t)$
0	0	0	d
0	1	1	0
1	0	0	1
1	1	d	0

(b) Clocked SR

State transitions		Required inputs
$Q(t)$	$Q(t + e)$	$T(t)$
0	0	0
0	1	1
1	0	1
1	1	0

(c) Clocked T flip-flop

State transitions		Required inputs	
$Q(t)$	$Q(t + e)$	$J(t)$	$K(t)$
0	0	0	d
0	1	1	d
1	0	d	1
1	1	d	0

(d) Clocked JK flip-flop

Synthesis: Simplification

- Find and simplifies h
 - Excitation: $Y = h(x, y)$
 - Select D

		x	
		0	1
$y_1 y_2$	00	00/0	01/0
	01	00/0	11/1
	11	01/0	10/0
	10	11/1	10/0

$Y_1 Y_2 / z$

State transitions		Required inputs D (t)
Q (t)	Q (t + e)	
0	0	0
0	1	1
1	0	0
1	1	1

(a) D flip-flop

Present State		Next State $X=0$		Next State $X=1$		Y_1 $X=0$	Y_1 $X=1$
y_1	y_2	y_1	y_2	y_1	y_2	D	D
0	0	0	0	0	1	0	0
0	1	0	0	1	1	0	1
1	1	0	1	1	0	0	1
1	0	1	1	1	0	1	1

Synthesis: Simplification (cont'd)

- Find and simplifies h
 - Excitation: $Y = h(x, y)$
 - Select D

		x	
		0	1
$y_1 y_2$	00	00/0	01/0
	01	00/0	11/1
	11	01/0	10/0
	10	11/1	10/0

$Y_1 Y_2/z$

State transitions		Required inputs $D(t)$
$Q(t)$	$Q(t + e)$	
0	0	0
0	1	1
1	0	0
1	1	1

(a) D flip-flop

Present State		Next State $X=0$		Next State $X=1$		Y_1 $X=0$	Y_1 $X=1$
y_1	y_2	y_1	y_2	y_1	y_2	D	D
0	0	0	0	0	1	0	0
0	1	0	0	1	1	0	1
1	1	0	1	1	0	0	1
1	0	1	1	1	0	1	1

		x	
		0	1
$y_1 y_2$	00	0	0
	01	0	1
	11	0	1
	10	1	1

$D_1 (= Y_1)$

Synthesis: Simplification (cont'd)

- Find and simplifies h for y_2

- Excitation: $Y = h(x, y)$
- Select D

		x	
		0	1
$y_1 y_2$	00	00/0	01/0
	01	00/0	11/1
	11	01/0	10/0
	10	11/1	10/0

$Y_1 Y_2 / z$

State transitions		Required inputs $D(t)$
$Q(t)$	$Q(t + e)$	
0	0	0
0	1	1
1	0	0
1	1	1

(a) D flip-flop

Present State		Next State $X=0$		Next State $X=1$		Y_2 $X=0$	Y_2 $X=1$
y_1	y_2	y_1	y_2	y_1	y_2	D	D
0	0	0	0	0	1	0	1
0	1	0	0	1	1	0	1
1	1	0	1	1	0	1	0
1	0	1	1	1	0	1	0

		x	
		0	1
$y_1 y_2$	00	0	1
	01	0	1
	11	1	0
	10	1	0

$D_2 (= Y_2)$

Synthesis: Simplification (cont'd)

- Find and simplifies h for y_1 and y_2
 - Excitation: $Y = h(x, y)$

		x	
		0	1
$y_1 y_2$	00	0	0
	01	0	1
	11	0	1
	10	1	1

$D_1 (= Y_1)$

		x	
		0	1
$y_1 y_2$	00	0	1
	01	0	1
	11	1	0
	10	1	0

$D_2 (= Y_2)$

		x	
		0	1
$y_1 y_2$	00	00/0	01/0
	01	00/0	11/1
	11	01/0	10/0
	10	11/1	10/0

$Y_1 Y_2/z$

$$D_1 = y_1 \bar{y}_2 + x y_2$$

$$D_2 = \bar{x} y_1 + x \bar{y}_1 = x \oplus y_1$$


Synthesis: Realization

- Output: $z = g(x, y)$
- Excitation: $Y = h(x, y)$

$$z = x\bar{y}_1y_2 + \bar{x}y_1\bar{y}_2$$


$$D_1 = y_1\bar{y}_2 + xy_2$$
 
$$D_2 = \bar{x}y_1 + x\bar{y}_1 = x \oplus y_1$$



Design a Counter

 - Design a synchronous bidirectional counter
 - Input $Up / \overline{Down}$ (Up)
 - $Up = 1 \Rightarrow$ Counting upward
 - $Up = 0 \Rightarrow$ Counting downward



Design a Counter: Step1

Present State			Next State $Up / \overline{Down} = 1$			Next State $Up / \overline{Down} = 0$			Flip Flops $Up / \overline{Down} = 1$			Flip Flops $Up / \overline{Down} = 0$		
Q_2	Q_1	Q_0	Q_2	Q_1	Q_0	Q_2	Q_1	Q_0	T_2	T_1	T_0	T_2	T_1	T_0
0	0	0	0	0	1	1	1	1			1			1
0	0	1	0	1	0	0	0	0			1			1
0	1	0	0	1	1	0	0	1			1			1
0	1	1	1	0	0	0	1	0			1			1
1	0	0	1	0	1	0	1	1			1			1
1	0	1	1	1	0	1	0	0			1			1
1	1	0	1	1	1	1	0	1			1			1
1	1	1	0	0	0	1	1	0			1			1

Design a Counter: Step1

Present State			Next State $Up / \overline{Down} = 1$			Next State $Up / \overline{Down} = 0$			Flip Flops $Up / \overline{Down} = 1$			Flip Flops $Up / \overline{Down} = 0$		
Q_2	Q_1	Q_0	Q_2	Q_1	Q_0	Q_2	Q_1	Q_0	T_2	T_1	T_0	T_2	T_1	T_0
0	0	0	0	0	1	1	1	1		0	1		1	1
0	0	1	0	1	0	0	0	0		1	1		0	1
0	1	0	0	1	1	0	0	1		0	1		1	1
0	1	1	1	0	0	0	1	0		1	1		0	1
1	0	0	1	0	1	0	1	1		0	1		1	1
1	0	1	1	1	0	1	0	0		1	1		0	1
1	1	0	1	1	1	1	0	1		0	1		1	1
1	1	1	0	0	0	1	1	0		1	1		0	1

Design a Counter: Step1

Present State			Next State $Up / \overline{Down} = 1$			Next State $Up / \overline{Down} = 0$			Flip Flops $Up / \overline{Down} = 1$			Flip Flops $Up / \overline{Down} = 0$		
Q_2	Q_1	Q_0	Q_2	Q_1	Q_0	Q_2	Q_1	Q_0	T_2	T_1	T_0	T_2	T_1	T_0
0	0	0	0	0	1	1	1	1	0	0	1	1	1	1
0	0	1	0	1	0	0	0	0	0	1	1	0	0	1
0	1	0	0	1	1	0	0	1	0	0	1	0	1	1
0	1	1	1	0	0	0	1	0	1	1	1	0	0	1
1	0	0	1	0	1	0	1	1	0	0	1	1	1	1
1	0	1	1	1	0	1	0	0	0	1	1	0	0	1
1	1	0	1	1	1	1	0	1	0	0	1	0	1	1
1	1	1	0	0	0	1	1	0	1	1	1	0	0	1

$$T_0 = 1$$

$$T_1 = (Q_0 Up) + \overline{Q_0} \cdot \overline{UP}$$


$$T_2 = (Q_0 Q_1 Up) + \overline{Q_0} \cdot \overline{Q_1} \cdot \overline{UP}$$

Design a Counter: Step1

$$T_0 = 1$$

$$T_1 = (Q_0 Up) + \overline{Q_0} \cdot \overline{UP}$$
 
$$T_2 = (Q_0 Q_1 Up) + \overline{Q_0} \cdot \overline{Q_1} \cdot \overline{UP}$$



Thank You



